

## FEATURES

14

Control Your Audio/Video Connections with the AVMux

24

Exploring the Vertical Blanking Interval

40

Employer Ownership of Employee and Consultant Work Product

# Control Your Audio/Video Connections with the AVMux

One of Steve's more popular Circuit Cellar projects from years ago was the AVMux. With today's more sophisticated home theater requirements and the availability of newer, better chips, it's time to revisit the AVMux project.

## FEATURE ARTICLE

Steve Ciarcia



about nine years ago, the concept of an entertainment (a.k.a., media) room

became a heavy topic in audiophile and videophile circles. Rec rooms lost their pool tables and pinball machines, and relatives expecting the same (free) spare bedroom were shown the Yellow Pages under "motels." Home builders who had just come to grips with jamming jacuzzis into the master bedroom closet now had to come up with a home theater to entice the sophisticated home buyer.

Aside from the physical room itself, the reality of a dedicated entertainment space was primarily a matter of assembling the components. Virtually all of the equipment (projection television, CD player, laserdisc, VCR, amps, etc.) was available off the shelf, but implementing the physical connections among the components presented a problem.

Virtually all of the equipment of sufficient quality for this purpose also had singular applications. Good stereo systems ("good" is interpreted as meaning audiophile quality) consisted of individual modules such as a tuner, preamplifier, amplifier, CD player, sound field processor, subwoofer amplifier, DAT player, and so forth. It was not uncommon to have to use eight or ten of these electronic subsystems to create the proper sound and video atmosphere in a true entertainment room.

The unfortunate truth back then was that while the concept of coordinated media was easily understood, an adequate means for channeling the audio and video signals among all

these subsystems that would ultimately result in the desired effect was no small task. In fact, it was a wiring maze. To ease the wiring congestion and simplify overall interconnection, I designed a combination 8x8 audio and video multiplexer.



Photo 1-The finished AV Mux and hand-held control unit add both sophistication and class to any home theater installation.

The AV Mux, as I called it, was (and is) exactly as the name implies. It was an electronic cross-matrix of switches which channels specific inputs to designated outputs. In the case of an 8x8 multiplexer, the inputs to it (commonly called the *froms*) come from the outputs of the various signal-generating subsystems, such as CD players, VCRs, laserdisc, tape recorders, and so forth (subsystems with both audio and video outputs would use the appropriate audio or video input side of the multiplexer). Similarly, the output side of the AV Mux was connected to the inputs of various other system components (called *tos*): preamplifier, amplifiers, surround decoder, soundfield decoder, tape recorders, and so forth.

Using the AV Mux and a series of push-button settings like "From 2 to 6" "From 3 to 5," and "From 3 to 7," would, for example, channel the laserdisc into a system combination of the preamp, amplifier, and subwoofer amp (we presume speakers are always connected to a particular amplifier). To change the source from the laserdisc to the CD player, we might enter "From 1 to 6" on the control. This "erases" the "From 2 to 6" connection and replaces it with "From 1 to 6" instead.

### A SOLUTION NOW LACKING A PROBLEM?

Nine years later, the scenario is quite different. Consumer audio and video equipment have made significant advances such that the borderline between true "audiophile" and "high-end" consumer quality is fuzzy at best.

To obtain superb sound and video in the past, the only solution was to use more expensive modules and externally connect things through an electronic multiplexer like the AV Mux.

Today, stereo manufacturers have succeeded in providing some real power and quality in a single enclosure. It is not hard to find the equivalent of the tuner, preamplifier, two 100-watt stereo amplifiers, subwoofer amplifier, a Pro-Logic surround decoder, and a dedicated audio/video multiplexer in one enclosure. A Mitsubishi unit I looked at recently included all this for \$1400. When I compare this to the \$10,000 I spent on the equivalent separate boxes.. .

AUX2 (remember, the tuner and surround decoder are already in the box, so they don't need external inputs), a simple push button or remote tells the internal multiplexer (frequently a relay) to channel the appropriate input through the preamp into the surround decoder and amplifiers. The outputs of this system are usually just speaker terminals and the direct video from the designated source. This video goes to a separate monitor such as a projection TV.

Depending upon the brand and the cost, you can find a variety of input/output configurations. Because they have a dedicated application, the audio multiplexer is always a Nx1 and the

The greatest attribute of today's "integrated component" single-box stereos [provided it is of sufficient quality] is that they contain an integral dedicated multiplexer. With external input designations like VCR1, VCR2, TAPE 1, TAPE2, CD, AUX1, and

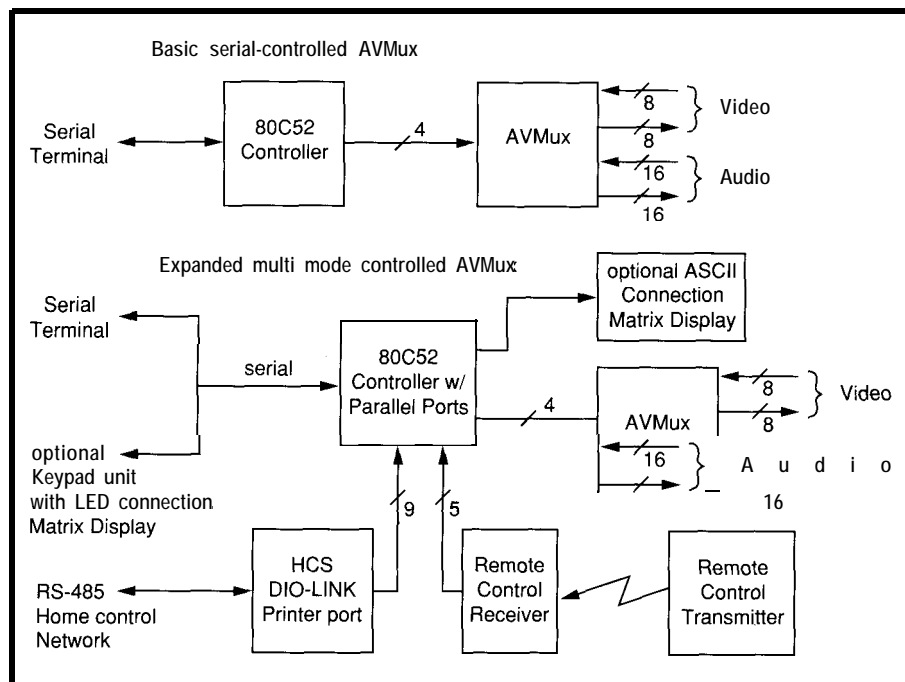


Figure 1-The AV Mux setup can be as simple as a serial terminal controlling it, or as complex as using wireless controls, user displays, and the HCS II to make a truly powerful system.

video rarely more than a 4x1 or 4x2. The Nx1 audio configuration is because all the amplifiers are in the one box. Any sound created in the system has to be amplified by this box and all speakers are wired to it. If there are eight audio inputs and only a single output that goes to the amps, then we have an 8x1 audio mux. Similarly, since this integrated system does not incorporate its own monitor, the manufacturers facilitate an external connection

through the mux. With four video sources and two outputs, we have a 4x2 video mux equivalent.

OK, enough beating around the bush. If you want to put together an entertainment room and you are on a limited budget, these integrated systems are the only way to go. One hundred watts channeled through efficient speakers can sound quite good in any room.

The problem comes when you want to do something that is not part of the basic box. The instant you want to connect three video inputs where you only have two available, change the front surround speaker power output capability from 20 W per

channel to 120 W per channel, or, using the same CD player, channel its output to a different set of speakers.

While the integrated system has greatly reduced the introductory cost of an entertainment room and satisfied bottom-up multiplexer execution to a great extent, it has done little for applications that don't fit the "mold."


As you might already have guessed, very little that I do fits any "mold." Let me explain.

Recently I decided to revamp our entertainment room. I thought of using an integrated surround system like those I described, but even the 350-W Mitsubishi unit didn't quite fit the bill. While it contained all the


right elements, it didn't have anywhere enough power and its internal switch multiplexer (or that on virtually any integrated unit) was far too limited for the I/O selection I have.

In all truth, if I didn't already have all the amplifiers and many of the subsystem components, I might would have changed the rules to fit the solution, but the disparity in performance was still there. My attitude toward surround sound movies is to create an environment as close to the pictured event as possible. When we watch Top Gun, only the lack of exhaust fumes and salt spray keeps you from actually believing you are on a carrier deck. To achieve this sound envelope requires considerably more than 5 W through a 6" x 9" oval TV speaker. In my opinion, it also takes more than the 300-400 watts available from the current top-of-the-line integrated units.

My entertainment room technique involves using separate modules (preamp, surround decoder, etc.) instead of the integrated unit. The fact that a stand-alone surround decoder/sound field processor has all its signal outputs available, gives me the option of using any size amplifiers I want. Being brief, let me just say that I'm using about 1200 watts on the dozen speakers comprising the surround system. Included among them is a pair of 200-W subwoofers that guarantee you don't miss an F-14 fly by.

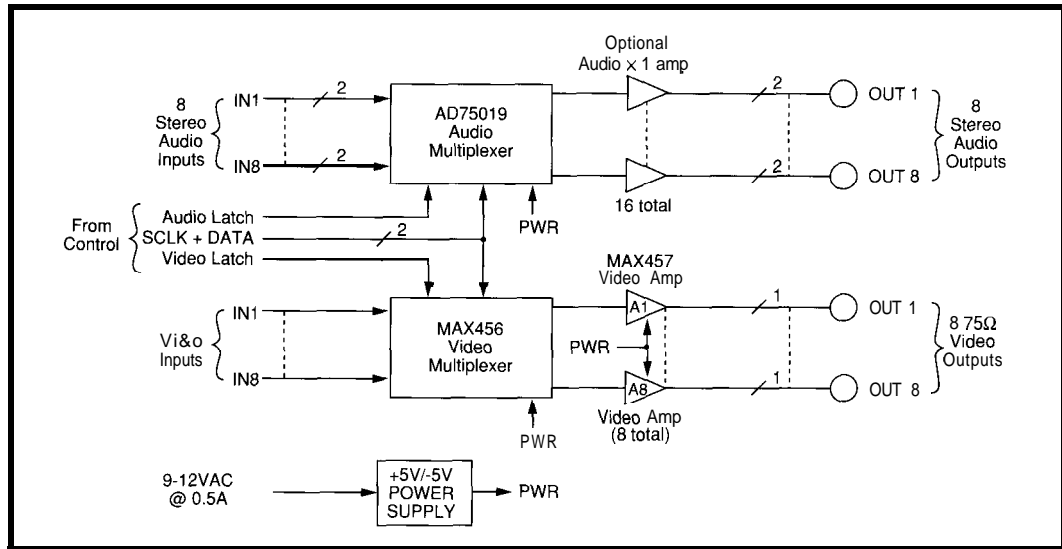

**Figure 2**—The Circuit Cellar VMux uses a pair of chips (one from Analog Devices and the other from Maxim) designed specifically for doing audio and video multiplexing.

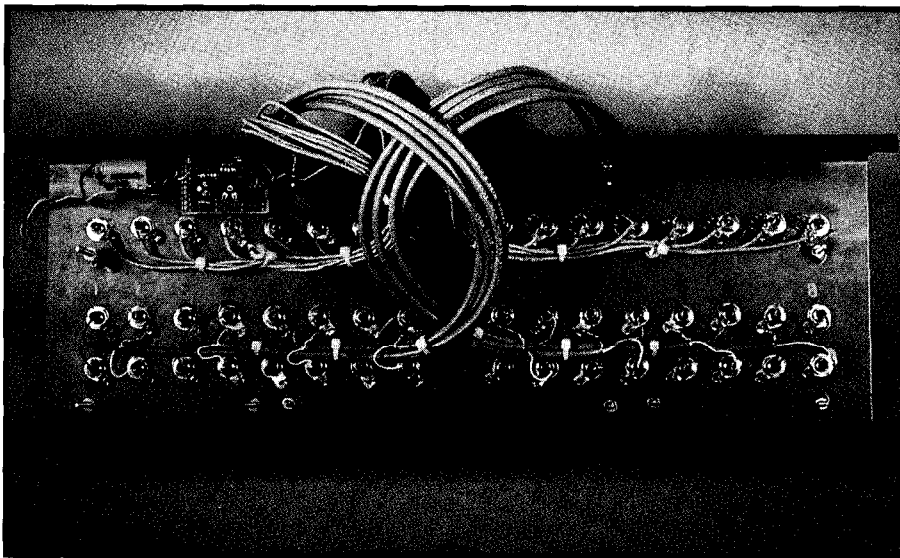

**Photo 2**—While the circuit isn't complex, wiring the project can be a major task since all the cables must be shielded.

What finally convinced me to redesign and further employ an external AVMux was the implementation of dual systems. I'm sure you've heard the saying, "If it ain't broke, don't fix it!" Well, that can apply to stereo systems as well.

Take away all the sound effects processing, decoding, and electronic signal manipulation and true sound quality of any stereo is simply an audio source, amplifier, and a pair of speakers. In my opinion, the sound produced by a pair of B&W 808


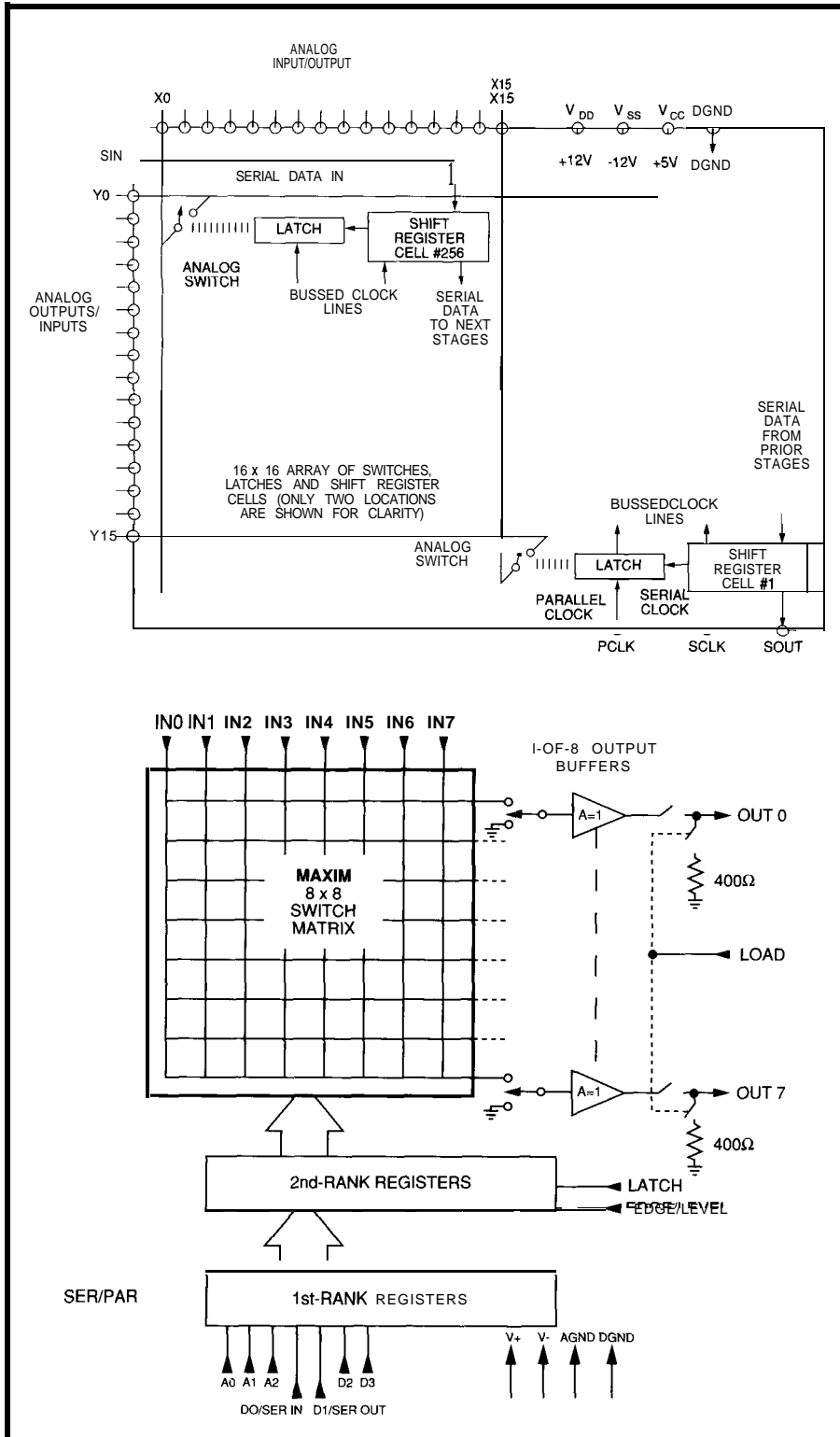


Figure 3-The Analog Devices AD75019 (top) is a 16x16 switch matrix ideal for use in audio applications while the Maxim MAX456 (bottom) is an 8x8 switch meant for video.

# RELAY INTERFACE

PROVIDES SOFTWARE CONTROL OF RELAYS

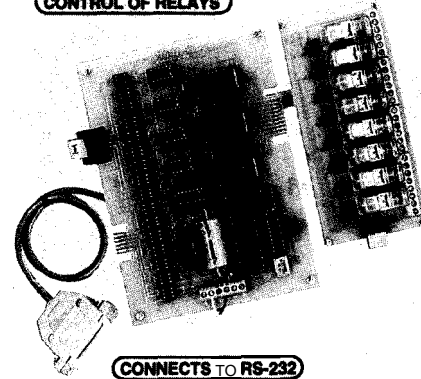


CONNECTS TO RS-232

AR-10 RELAY INTERFACE (16 channel).....\$ 89.95  
 Two 8 channel (TTL level) outputs are provided for connection to relay cards or other devices (expandable to 128 relays using EX-16 expansion cards). A variety of relays cards and relays are stocked. Call for more info.  
 AR-2 RELAY INTERFACE (2 relays, 10 amp).....\$ 44.95  
 RD-8 REED RELAY CARD (8 relays, 10 VA).....\$ 49.95  
 RH-8 RELAY CARD (10 amp SPDT, 277 VAC).....\$ 69.95

# ANALOG TO DIGITAL

8, 10 & 12 BIT RESOLUTION

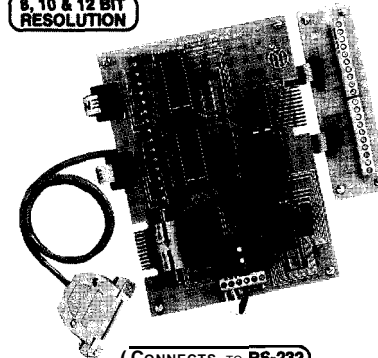

CONNECTS TO RS-232

ADC-16 AID CONVERTER\* (16 channel/8 bit)...\$ 99.95  
 ADC-8G AID CONVERTER\* (8 channel/10 bit)...\$124.90  
 Input voltage, amperage, pressure, energy \*saga, joysticks and a wide variety of other types of analog signals. RS-422/RS-485 available (lengths to 4.W). Call for info on other A/D configurations and 12 bit converters (terminal block and cable sold separately).  
 ADC-8E TEMPERATURE INTERFACE\* (8 ch)...\$ 139.95  
 Includes term. block & 8 temp. sensors (-40' to 146' F).  
 STA-8 DIGITAL INTERFACE\* (8 channel).....\$ 99.95  
 Input on/off status of relays, switches, HVAC equipment, security devices, smoke detectors, and other devices.  
 STA-8D TOUCH TONE INTERFACE\*.....\$ 134.90  
 Allows callers to select control functions from any phone.  
 PS-4 PORT SELECTOR (4 channels RS-422).....\$ 79.95  
 Converts an RS-232 port into 4 selectable RS-422 ports.  
 CO-485 (RS-232 to RS-422/RS-485 converter).....\$ 44.95

● EXPANDABLE...expand your interface to control and monitor up to 512 relays, up to 576 digital inputs, up to 126 analog inputs or up to 126 temperature inputs using the PS-4, EX-16, ST-32 & AD-16 expansion cards.

FULL TECHNICAL SUPPORT...provided over the telephone by our staff. Technical reference & disk including test software & programming examples in Basic, C and assembly are provided with each order.

HIGH RELIABILITY...engineered for continuous 24 hour industrial applications with 10 years of proven performance in the energy management field.

CONNECTS TO RS-232, RS-422 or RS-485...use with IBM and compatibles. Mac and most computers. All standard baud rates and protocols (50 to 19,200 baud).

Use our 800 number to order FREE INFORMATION PACKET. Technical information (614) 464-4470.

24 HOUR ORDER LINE (800) 842-7714  
 Visa-Mastercard-American Express-COD

International & Domestic FAX (614) 464-9556  
 Use for information, technical support & orders.  
 ELECTRONIC ENERGY CONTROL, INC.  
 360 South Fifth Street, Suite 604  
 Columbus, Ohio 43215-5436

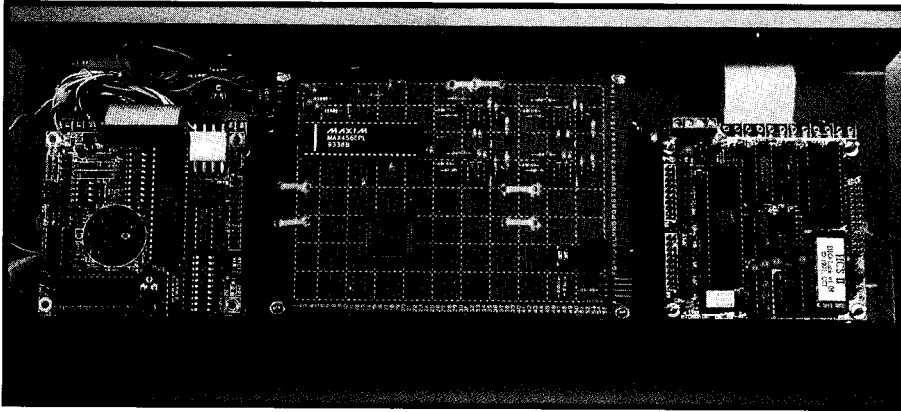


Photo 3—Inside the finished AVMux you can see the controller (left), multiplexer electronics (center), and HCS II DIO-Link (right).

Reference Speakers [running at another 1200 watts) comes close to perfect audio. I like classical music straight, while rock music seems better with all the effects. That means I have one system configuration for classical and a completely different one for rock.

Keeping a dual redundant system like this requires a sophisticated multiplexer to allow a common set of AV sources to be routed among all input combinations.

## A SIMPLE MUX DESIGN WITH MANY OPTIONS

The new AVMux has improved performance primarily because it uses newer technology. Like the original unit, this is an 8x8 stereo audio and 8x8 video multiplexer. Unlike its predecessor, however, this mux allows the user to select independent or coordinated control of the audio and video sections. You can have eight audio sources with only three corresponding video signals and still use the other five video inputs for unrelated activities. Audio and video channels can be routed independently.

Due to its particular architecture, which allows independent audio and video operation, you can choose to make just a video-only or audio-only multiplexer. Control is realized with an 80C52-based microcontroller which allows considerable expansion options. As outlined in Figure 1, the new Circuit Cellar AVMux can operate through simple, direct, serial RS-232 control; operate with a wireless infrared remote control; operate with a hand-held keypad and LED connection matrix display; display an ASCII list of

connected points during operation; and allow network connection (using a DIO-Link) with functional control provided by the Circuit Cellar HCS II.

As you can see, this is a long list of functions. It also incorporates features that involve considerably more software than I cared to write. To finish in a reasonable time, I drafted Jeff Bachiochi to help. I'm glad I did and I'd further have to say that this new AVMux has as many features as it does because of his added expertise. Since we worked together, Jeff will be covering certain AVMux aspects in his column as well.

For this month, I'll describe the basic AVMux components and the controller design. Next month, Jeff will fill in more on how the software works, with particular emphasis on the remote keypad/LED connection matrix unit. I'll conclude next month with the wireless remote control interface specifics.

## NEW SINGLE-CHIP MULTIPLEXERS

Any rational person would not even attempt to make an 8x8 multiplexer if it were not for the availability of some new highly integrated multiplexer chips from Analog Devices and Maxim. The configuration of the basic AVMux using these chips is outlined in Figure 2. Regardless of all the other optional features, this basic circuit stays the same. The two sections—audio and video—are also divisible and you could build each separately.

The audio multiplexer is the simpler of the two, both in concept and construction. Employing an

Analog Devices CMOS AD75019 16x16 crosspoint switch array (its functional block diagram is in Figure 3) allows the complete circuit to be fabricated with just that single chip.

Unlike its video companion, an 8x8 stereo audio multiplexer involves switching 16 signals (8 left channel and 8 right channel). I chose the AD75019 specifically so I would not have to use two 8x8 devices. The AD75019 contains 256 analog switches in a 16x16 array. Any of the X or Y pins may serve as inputs or outputs. Any of the X pins can be programmed to connect to any Y pins and vice versa. The switches allow amplitudes up to the supply voltages and have a typical resistance of 150 ohms.

Figure 4 shows the actual circuit connections. To keep things simple, we designated all X pins as inputs and all Y pins as outputs: X0-X7 are right channel inputs 1-8, X8-X15 are left channel inputs 1-8, Y0-Y7 are right channel outputs 1-8, and Y8-Y15 are left channel outputs 1-8. I know that chip designations use "0" instead of "1" as the first signal line, but try to tell someone unfamiliar with electronics that and you'll get a blank stare. Zero to seven is for the builder and one to eight is for the user.

Connecting input X2 to output Y7 is accomplished by closing the crosspoint switch at their intersection. Each of the 256 crosspoint switches is controlled by a shift register cell. If the cell contains a 0, the switch is open. If the cell contains a 1, the switch is closed. The contents of all the cells, describing the crosspoint matrix map, is a 256-bit data packet.

The data is loaded serially via the SIN input (DATA) and clocked into the 256-bit shift register via SCLK (CLK). When all 256 bits have been entered, data is transferred in parallel to the switch latches on the high-to-low leading edge transition of PCLK (ALD). One caution to note here: the serial shift register in the AD75019 is dynamic and the minimum clock rate is 20 kHz (the maximum rate is 5 MHz). With a high-level language controller, an assembly language routine is often used to send data to

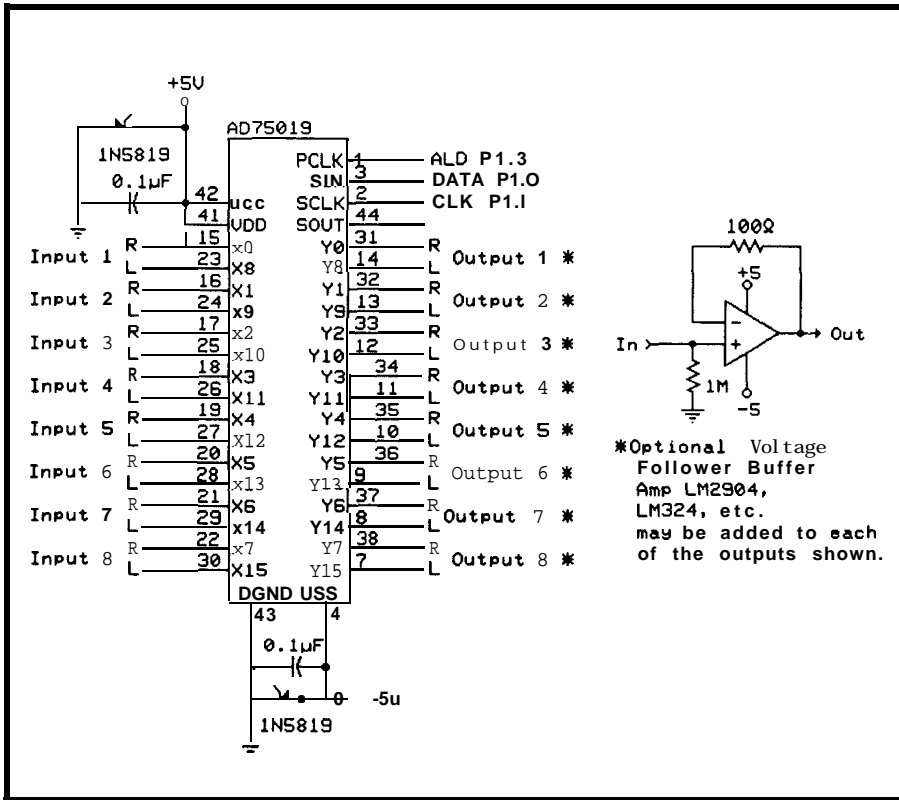


Figure 4—The actual connections to the AD75019 are numbered 1-8 rather than 0-7 to make it easier on the user.

this chip. Once programmed, however, operation is static and the switches stay programmed for as long as the power is on.

One final note on this chip. When powered on  $\pm 5$  V, the AD75019 has a typical switch resistance of 300 ohms. Many applications may be unaffected by this added resistance and you can use the circuit as is. If you are unsure or desire extra output protection, add the voltage follower buffer amplifier to each output channel (16 amps total) as noted in the schematic.

### A NEW MAXIM MULTIPLEXER

If you look closely at the spec sheet on the AD75019, you'll note that it has a switch frequency response of 20 MHz. While I could have used it for both sections, I opted to use a chip specifically designed for video.

I decided to make the AVMUX video section using the new Maxim MAX456 CMOS 8x8 crosspoint switch (functional block diagram in Figure 3) specifically designed for video. It contains a similar register, latch, and switch arrangement as the audio mux, but the MAX456's connection logic prohibits illegal switch connections.

The MAX456 is an 8x8 matrix, and there are indeed 64 separate switches, but in video applications, not all crosspoint connections are allowed. Video outputs should not be tied together, for example.

In the MAX456, each output connection command is thought of as a combination of the binary address of the selected 1-of-8 inputs and data such as whether the buffer is on, off, or grounded. This data combination results in a 4-bit value for each output channel. To program 8 channels, therefore, only requires 32 bits.

The MAX456 is unique in that it can load this switch register data by either parallel or serial means. To keep programming consistency, I chose the latter. The 32 bits are applied to the DO/SER IN (DATA) line as the  $\bullet$  WR (CLK) line is clocked (these are the same two lines that are connected to the audio mux). At its conclusion, the data is latched on a high-to-low leading-edge transition of the LATCH pin (VLD). Using common data and clock control lines with separate video load (VLD) and audio load (ALD) allows just four control lines to control the whole AVMUX.

# \$149 ICE?!!!

Yes, that's right! HTE has dropped the price of its popular 8031/32 Enhanced DryICE from \$269 to \$149. Now you can't afford to be without one! This ICE performs single step, real-time execute to breakpoint, disassembly and more. 8K user code space, expandable to 32K. Order yours today!

## More ICE

Our DryICE Plus has so many features, the price is unbelievable. 48K of user code space, real-time execution, and expandability to nearly all of the 8051 family processors. We are now supporting pods for the 803112, 8751, 80CL51/32, 8051Fx, 80C154, 80C410/1, 80C451, 80C528, 80C550, 80C535, 80C537, 80C552/562, 80C575, 80C652, 80CL781/2, and 80C851. With pod\$ priced at only \$149, going to a different, higher integration processor is easy. Pod and base unit are just \$446 complete!

## Controller 80C552

At \$149, our 552SBC-10 OEM board has the price and features you need right now! It's an 8051 core processor with an eight channel, 10-bit A/D, two PWM outputs, capture/compare registers, 16 digital I/O, one RS232 serial port, four JEDEC memory sockets. Add options like two more RS232/422/485 ports, 24 more digital I/O, real-time clock, serial EEPROM, and battery-backup for clock and RAM. Start with the Development board; all the peripherals and a debug monitor for only \$349. Download and debug your code, assembly or 'C', right on the SBC, then use the low-cost OEM board of your choice for production. We also do customs - call for a free quotation.

## 80C188 SBC

MEW! Starting at only \$249. Two serial RS232/422/485, Parallel, expand to 16 ch. 12-bit A/D, 8 ch. 12 bit D/A, Keybd, \_CD, Relay I/F, more. Call for details!

Call for your custom product needs.  
Quick Response



HiTech Equipment Corp  
9400 Activity Road  
San Diego, CA 92126  
[FAX: (619) 530-1458]

(619) 566-1 892

70662. 1241 @compuserve.com

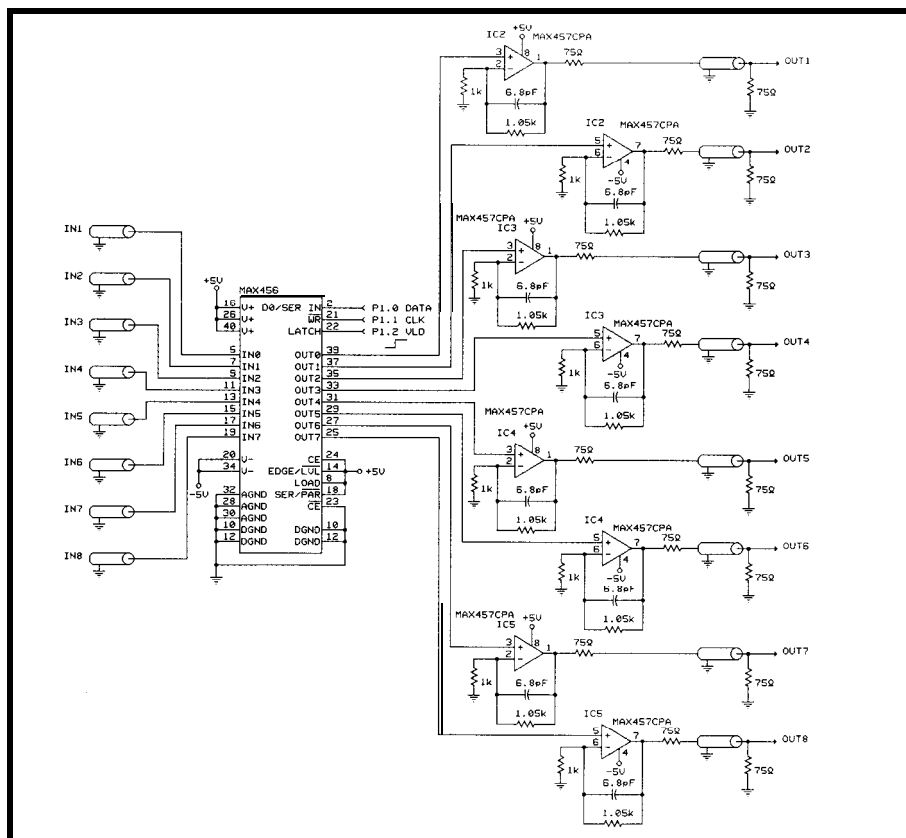


Figure 5—While the circuitry around the MAX456 video mux is simple, having to use shielded cable complicates wiring. The MAX457 video amps are used for impedance matching.

One additional note on the MAX456. While it does have internal video buffers, they can only drive 400-ohm loads. Since most video applications require 75-ohm impedance, additional external buffer amplifiers have to be added. The dual-amp MAX457, which has a 70-MHz unity-gain bandwidth, is the perfect choice. As connected in Figure 5, the MAX457 is configured for a closed-loop gain of 2. The gain selection resistor is set at 1.05k instead of 1k to make up for open-loop gain loss. The 6.8-pF capacitor helps eliminate phase delay at high frequencies.

We have to be careful to properly match the cable impedances even in a hand-wired prototype. This particular circuit allows us to drive a doubly terminated 75-ohm line. The combination of the series 75-ohm resistor and the 75-ohm termination at the output connector produces a low-noise 75-ohm external connection with the appearance of unity-gain amplification.

## A FAMILIAR CONTROLLER FOR THE AVMUX

As I mentioned, it takes just 4 wires from the controller to the AVMUX chips to do everything. Figure 6b is an 80C52-BASIC-based microcontroller circuit which is more than adequate for the task. Together, they represent the configuration outlined in Figure 1. I used a Micromint RTC52 and RTCIO as the controller rather than spending the time and effort to build one. At the price I get them, it wasn't a hard choice.

We chose to use BASIC (with assembly language calls) here because this is not a speed-intensive control application. Using a high-level language also expedited development and made certain expansion options easier. For example, since BASIC-52 supports a serial printer output, presenting an ASCII connection list for terminal display was as easy as adding an LPRINT (PRINT#) command.

The controller circuit has two sections: basic controller with one serial port and one parallel port (Figure 6a), and the same basic configuration with more parallel ports and nonvola-

## Video Frame Grabber


- \$495 Including Software with "C" Library
- Half Slot Card for Compact Applications
- Real Time Imaging with Display Output
- 8 Bit (256 Gray Levels)

### FEATURES:

- Single 512 X 484 Image or Four 256 X 242 Images
- External Trigger
- Input Look Up Table
- Low Power Option Available
- Elegant Software Interface
- <10 nsec Pixel Jitter Means Accurate Digitization
- EISA (PC) Bus and STD Bus Products Available
- RS-170 and CCIR Video Formats Available
- Binary and TIFF File Formats

The Cortex I is used in machine vision, industrial control, medical, security and scientific applications around the world.

ImageNation strives to delight customers with quality products and personal service at a competitive price.

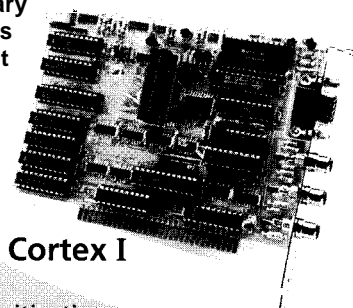

Cortex I

Call today for volume pricing or to discuss your application.

**ImageNation Corporation**  
Providing Imaging Solutions  
FAX (503) 643-2458 • (800) 366-9131

P.O. Box 276  
Beaverton, OR 97075  
(503) 641-7408

tile memory (Figures 6a and 6b). Since this circuit has been presented on numerous occasions, I will not belabor it. The initial circuit is suitable for operating the AVMux through a serial terminal. A simple connection display and command menu prompts the user to designate the desired From-To connections. More later.

## PROTOTYPING

Success here is not just a function of interpreting the schematic correctly. Experience counts.

As you can see from the photos, even though this is only a six-chip circuit, it is a wiring nightmare. To keep signals from radiating or picking up the radiation from adjacent signals, all input and output wires should be shielded cable [now you might understand the reason for doubly terminated video buffers). I even used shielded cable from the MAX456 to the buffer amps. The enclosure should be metal to serve both as an EM1 shield and as a large noise-reducing common ground. It can also function as the heatsink for your power supply.

Ordinarily, I wouldn't discuss the power supply in any detail. In an application where limiting electrical noise is critical, I believe it a noteworthy exception. First of all, I suggest

you use a linear supply only and not a switching regulated unit. Without the benefits of printed circuit board layout, ground planes, single-point termination, and proper shielding (all of which are incorporated in a production unit), a switching power supply is just another source of unwanted noise (herringbone pattern on the video and buzz in the audio).

Getting from here to there can be an interesting journey, however. I designed my AVMux as a totally enclosed unit. My intention was to use one of those cheap wall-module power sources and an internal regulator. The AVMux operates on +5 V and -5 V. Unfortunately, all the cheap wall-modules seemed to be 2-wire output.

Since I couldn't just throw in a switching regulator or charge pump inverter to get -5 V, I concluded that my only option was an elaborate dual tracking regulator with a concocted ground. Would I have to resort to an external power supply and pipe everything in instead?

The answer turned out to be really low tech. Shown in Figure 7, the AVMux power supply is just a regulated-output AC-to-DC converter. We can get by with a 2-wire voltage source if it is AC. The AC is then half-wave rectified and stored as separate positive


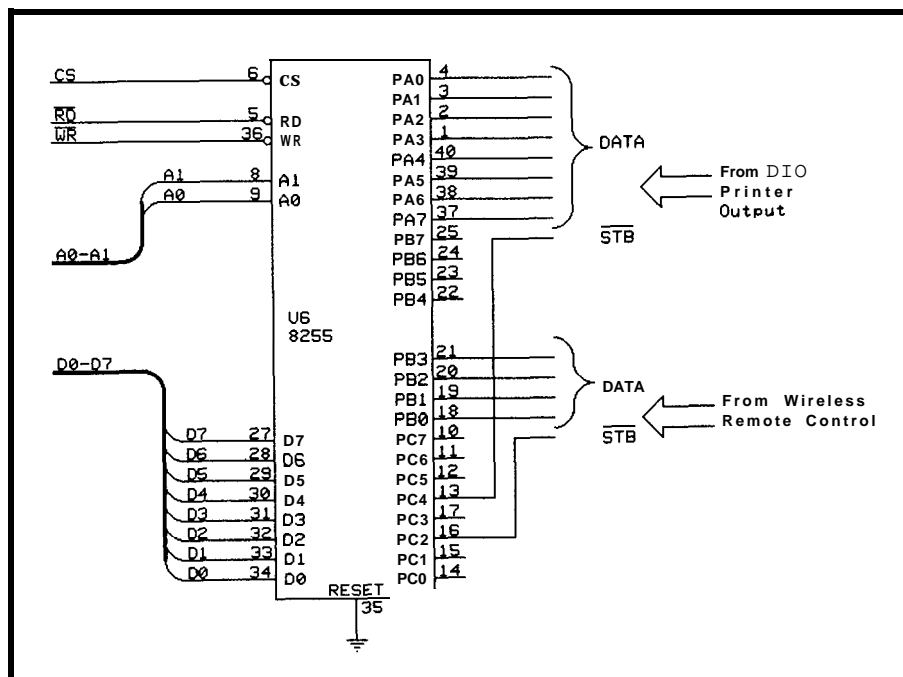


Figure 6a—To add either HCS II or wireless remote control to the AVMux, an 82C.55 must be added to the core controller in Figure 6b.

# NEW Data Acquisition Catalog

Covers expanded line.

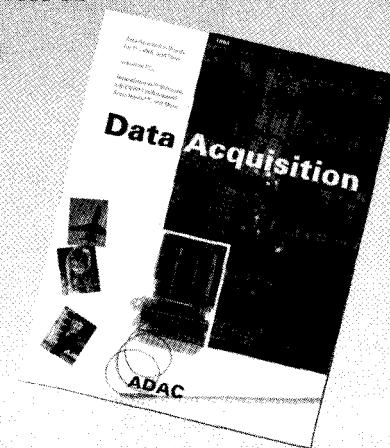

**FREE!**

1994 120 page catalog for PC, VME, and Qbus data acquisition. Plus informative application notes regarding anti-alias filtering, signal conditioning, and more.

NEW Software:  
**LabVIEW<sup>®</sup>**, **LabWindows<sup>®</sup>**,  
**Snap-Master<sup>™</sup>**, and more

NEW Low Cost I/O Boards

NEW Industrial PCs

NEW **Isolated** Analog and Digital Industrial I/O

New from the inventors of plug-in data acquisition.

Call, fax, or **mail** for your free copy today.

## ADAC

American Data Acquisition Corporation  
 70 Tower Office Park, Woburn, MA 01801  
 Phone: (800) 648-6589 Fax: (617) 938-6553



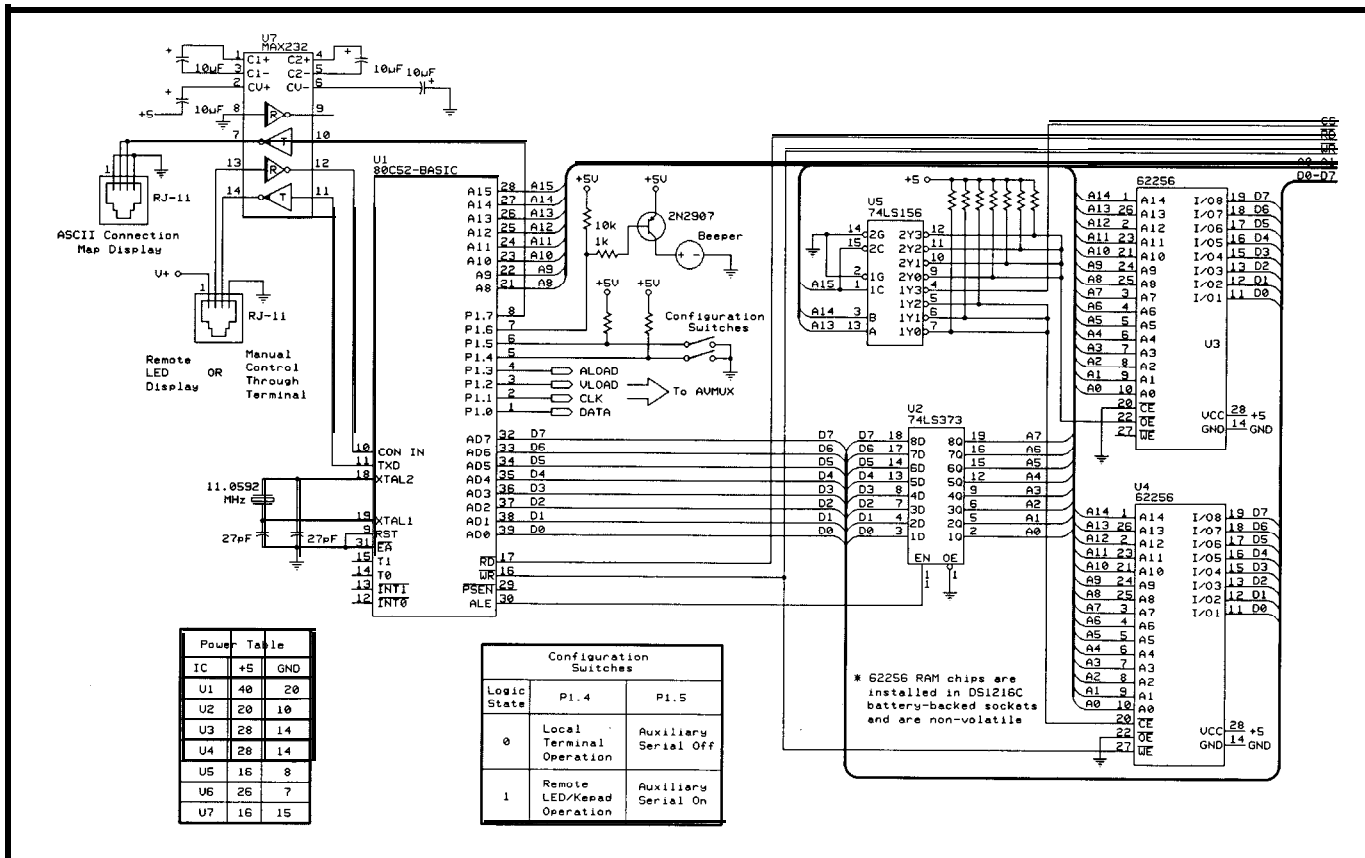


Figure 6b—The control section of the AVMuX uses the same 80C52-BASIC core seen in many other projects. Connections to the outside world are done through RJ11 jacks

and negative supplies with a common ground. Two three-terminal regulators simply convert this to +5 V and -5 V, respectively. The one notable circuit peculiarity is that each regulator has been configured for voltage output adjustment with a pot. By referencing these pots to the opposite supplies, the overall input-output differential necessary for these three-terminal regulators is reduced. Rather than a 12-VAC input, a 9-VAC will work just fine. The benefit is reduced power dissipation and a cooler AVMuX box.

### AVMUX OPERATION

The AVMuX is designed to operate in a variety of modes. With just the basic serial controller, all user interaction is through a terminal. When initialized, the program displays a connection matrix. To set a connection, the user designates whether it is (A)udio, (V)ideo, or (B)oth. Answering (A) displays the audio matrix while (V) or (B) displays the video matrix. The next entries are the From and To channel numbers, or cancel. The program then repeats the display,

showing it with the new connections (Jeff's program is on the Circuit Cellar BBS for anyone building the AVMuX).

As I mentioned, by using BASIC we have a serial printer output also available. One program function physically documents the entire From-To connection list, by component names (such as From ADS CD Player To Nakamichi Preamp Aux 2 input). This is for people who don't want to carry a component list to remember channel numbers or for those who want to have space in their stereo cabinet and want a unique terminal display.

### EXPANDING AVMUX FEATURES—THE HCS CONNECTION

Adding the 8255 PPI to the basic controller circuit facilitates other AVMuX features. Initial operation is through a serial ASCII terminal. Considering that the communication is simply the 12 characters typically on a telephone keypad, other methods can be employed to communicate these characters.

The first option we thought of was a hand-held remote that presented a display of the connected channels on an 8x8 LED array. It also had an integral keypad to enter commands.

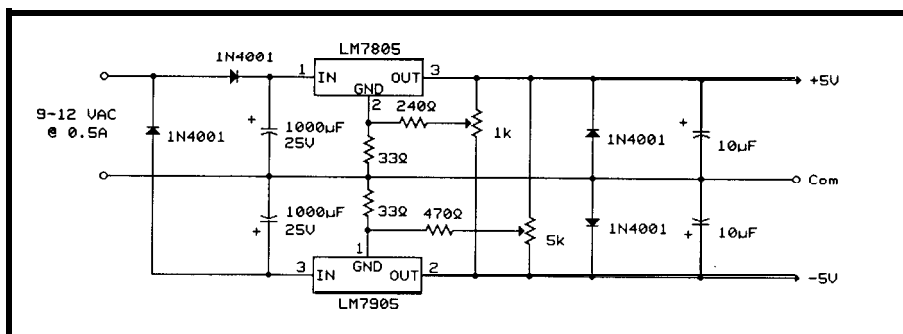


Figure 7—The power supply section creates quiet positive and negative supplies for the amplifiers from an AC source.


# RICE16-5x

This construction of this unit and a description of its software will be presented by Jeff next month.

The next brain storm we had was to connect the AVMux so it could work independently from, or in conjunction with, the HCS II and the trainable infrared MCIR-Link. The connection is accomplished using the DIO-Link.

Normally, the DIO-Link is used as an 8-bit, bit-programmable I/O port on the HCS II's RS-485 network. The DIO-Link can also be set to drive a parallel printer. In this configuration, all bits are outputs and each character transfer is accompanied by a strobe pulse. Character transfer timing is programmable within the DIO-Link.

Port A and one bit of Port C are used to receive the parallel data. The HCS can command the AVMux by simply sending an ASCII string, such as "A35" (make an Audio connection from 3 to 5), to the DIO-Link printer port. It's as easy as that.

Since we were accepting parallel data inputs anyway, it didn't seem outrageous to consider an additional source. The total 12-character vocabulary could also be represented as 12 combinations within a 4-bit code. It shouldn't be too hard to communicate these codes using readily available remote control transceiver chips. In fact, next month I'll demonstrate such a wireless remote interface design. 

*Steve Ciarcia is an electronics engineer and computer consultant with experience in process control, digital design, and product development. He may be reached at [steve.ciarcia@circellar.com](mailto:steve.ciarcia@circellar.com).*


## SOURCE

Some components of this project may be purchased from

Pure Unobtainium  
13109 Old Creedmoor Rd.  
Raleigh, NC 27613  
Phone/fax: (919) 676-4525
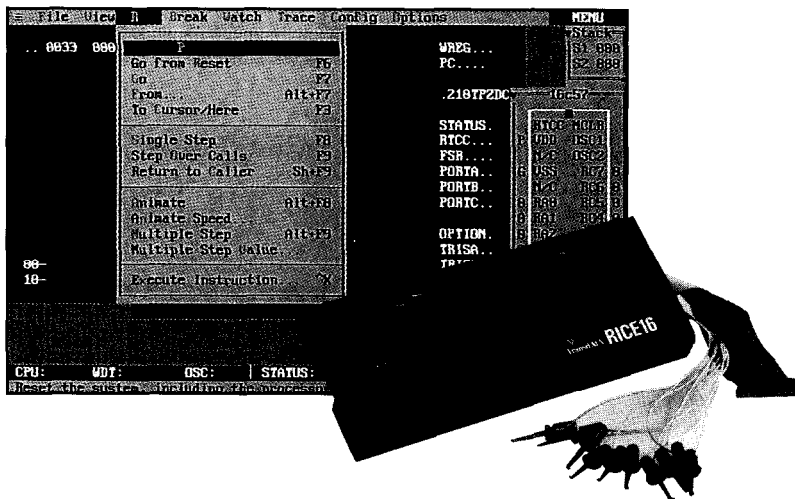
## IRS

401 Very Useful  
402 Moderately Useful  
403 Not Useful




## Real-Time Emulation to 16MHz

Complete system for **16C5x** only \$895.00'

Introducing RICE16-5x, real-time, non-intrusive in-circuit emulator for the PIC16C5x family microcontrollers: a feature-filled development system at an affordable price. \* Suggested Retail for US only

- Real-time Emulation to 16MHz
- Non-intrusive Operation
- PC-Hosted via Parallel Port
- 8K Program Memory
- 8K deep by 24 bits wide Trace Memory
- Source Level Debugging
- Unlimited Breakpoints
- External Trigger Break with either "AND/OR" with Breakpoints
- Trigger Outputs on any Address Range
- 12 External Logic Probes
- User-Selectable Internal Clock from 40 frequencies or External Clock
- Easy-to-use windowed software
- Single Step, Multiple Step, To Cursor, Step over Call, Return to Caller, etc.
- Search Capability in Source Code, Program Memory and Trace Buffer
- On-line Assembler for Patching Instruction
- Support; 16C71 and 16C84 with Optional Interchangeable Probe Cards
- Comes Complete with TASM16 Macro Assembler, Windowed Software, Power Adapter, Parallel Adapter Cable and User's Guide
- 30-day Money Back Guarantee
- Made in the U.S.A.

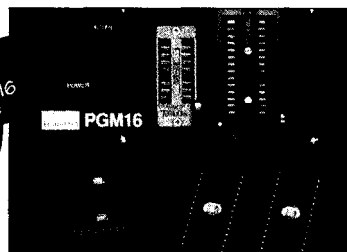Call our BBS at (214)980-0067 to download DEMO:RICE16.ZIP



\* for a limited time only



Advanced Transdata Corporation Tel (214) 980-2960  
14330 Midway Road, Suite 104, Dallas, Texas 75244 Fax (214) 980-2937